

Resistance

Created: Wednesday, 31 August 2011 07:59 | Published: Wednesday, 31 August 2011 07:59 | Written by Super User | Print

Introduction to Resistance




The current flowing through a conductor encounters some obstruction to the current.

This obstruction is called electrical resistance. Every material has some **electrical resistance** and is the reason that the conductor gives out heat when the current passes through it. Energy is used up as the voltage across the component drives the current through it, and this <u>energy</u> appears as heat in the component.

Special components called resistors are made for the express purpose of creating a precise quantity of resistance for insertion into a circuit. They are typically constructed of metal wire or carbon, and are engineered to maintain a stable resistance value over a wide range of environmental conditions.

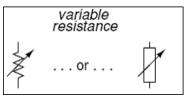The most common schematic symbol for a resistor is a zig-zag line:





Resistors can also be symbolized as having varying rather than fixed resistances. This might

be for the purpose of describing an actual physical device that is designed to provide an adjustable resistance, or it could be to show some component that just happens to have an unstable resistance:

The electrical resistance of a circuit component or device is defined as the ratio of the voltage applied to the electric current which


flows through it:
$$R = \frac{V}{I}$$

We need resistance to reduce the flow of electrons through a circuit, so we can build resistors to provide electrical resistance

Unit of Resistance

Resistance is measured in ohms, and the symbol for ohm is the omega?.

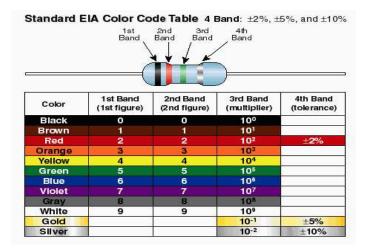1? is quite small for electronics so resistances are often given in k? and M?.



1 k? = 1,000?, and 1 M? = 1,000,000?.

Resistors used in electronics can have resistances as low as 0.1? or as high as 10 M?.

Reading Resistor Values

The resistance of resistors is indicated using color-coded bands on the body of the resistor. The first three color bands indicate the value of the resistor in ohms.

Resistors connected in a series

When resistors are connected in a series their combined resistance is equal to the individual resistances added together. For example if resistors R1 and R2 are connected in a series their combined resistance, R, is given as follows:

$$R_1$$
 R_2 R_n

Combined resistance in a series: R = R1 + R2


This can be extended for more resistors: $\mathbf{R} = \mathbf{R1} + \mathbf{R2} + \mathbf{R3} + \mathbf{R4} + \dots$

Resistors connected in parallel

When resistors are connected in parallel their combined resistance is less than any of the individual resistances. There is a special equation for the parallel combination of the resistance of two resistors R1 and R2.

The combined resistance of two resistors in parallel:

$$R = \frac{R1 \times R2}{R1 + R2}$$

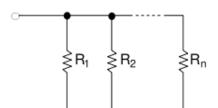

For more than two resistors connected in parallel, a more difficult equation must be

used. This adds the **reciprocal** ("one over") of each resistance to give the **reciprocal** of the combined resistance, R:

1/R = 1/R1+1/R2+1/R3+-----

The simpler equation for two resistors in parallel is much easier to use!

Want to know more about resistance? Click here to schedule a live session with an eAge eTutor!

About eAge Tutoring:

<u>eAgeTutor.com</u> is the premium online tutoring provider. Using materials developed by highly qualified educators and leading content developers, a team of top-notch software experts, and a group of passionate educators, eAgeTutor works to ensure the success and satisfaction of all of its students.

Contact us today to learn more about our guaranteed results and discuss how we can help make the dreams of the student in your life come true!

Reference links:

- http://www.en.wikipedia.org/wiki/voltage
- http://www.en.wikipedia.org/wiki/energy
- http://hyperphysics.phy-astr.gsu.edu/hbase/electric/elecur.html#c1

Category:ROOT

Joomla SEF URLs by Artio